

NORTON ANALYSIS

Will



Practice Questions

NORTON'S THEOREM

①


It states that any two terminals of a network can be replaced by an equivalent current source and an equivalent parallel resistance.

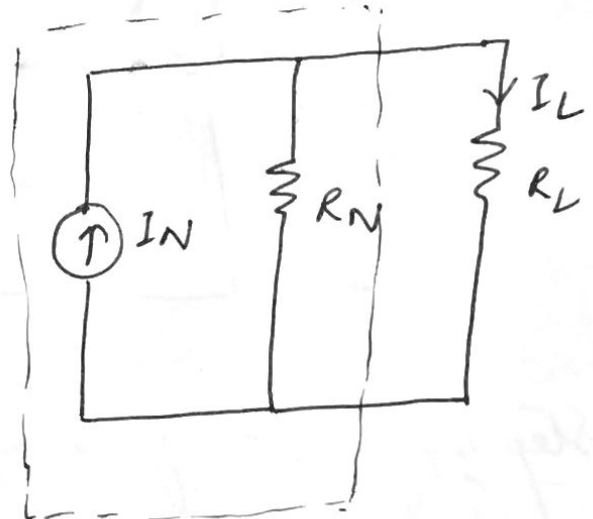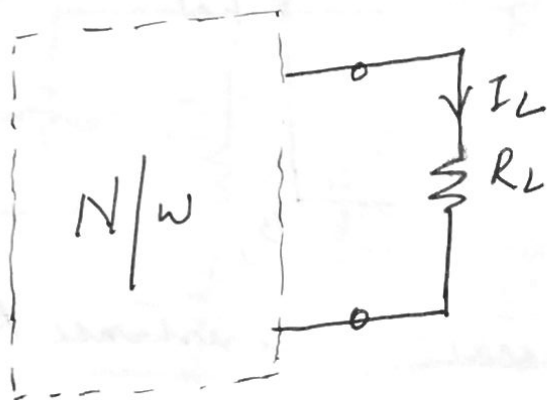- The constant current is equal to the current which would flow in a short circuit placed across the terminals.
- The parallel resistance is the resistance of the N/w when viewed from these open ckt terminals.




Norton's
N/w

EXPLANATION

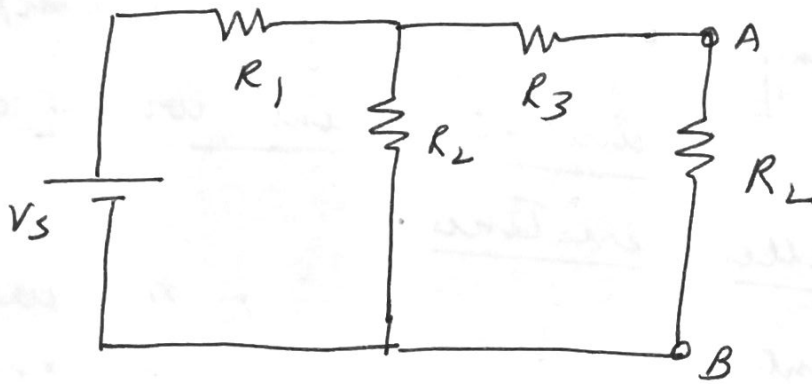


⇒ Find the current through R_L

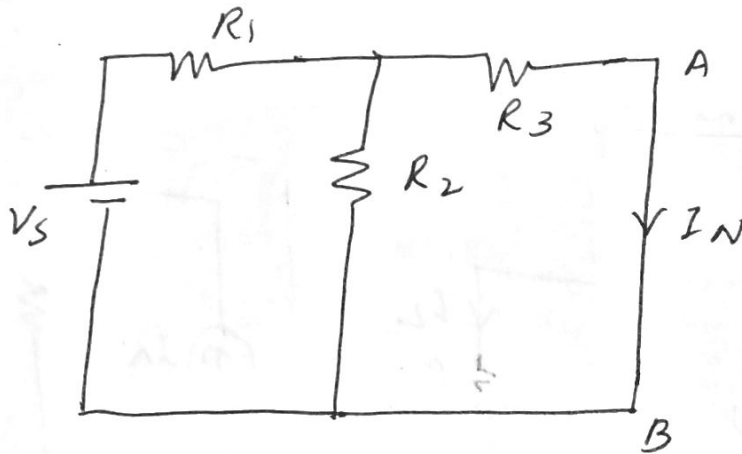Step I:- Remove the load resistor R_L from the N/w and calculate short ckt current I_{SC}



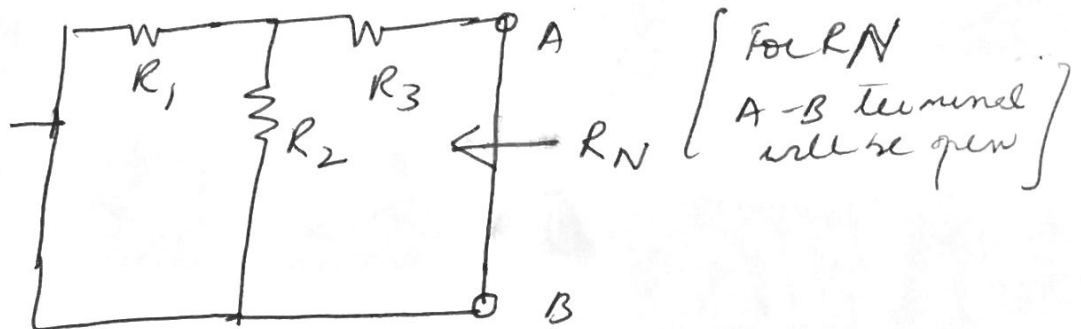
Step II:- For finding parallel resistance R_N , replace voltage source by short ckt



$$R_N = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

Step 3 Draw Norton's equivalent ckt.


(2)

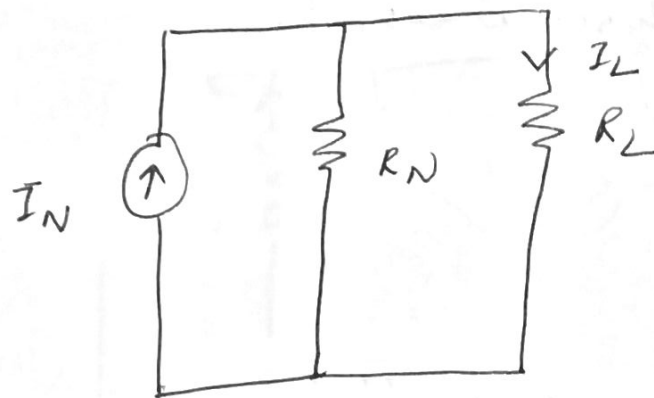


[acc to current divider rule]

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

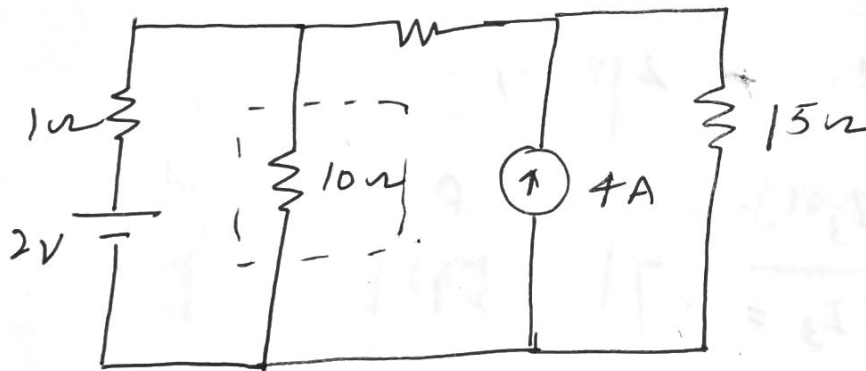Numerical 1 :- Find the current through 10Ω resistor using Norton's analysis.



Step 1 :- Short ckt the given resistor.

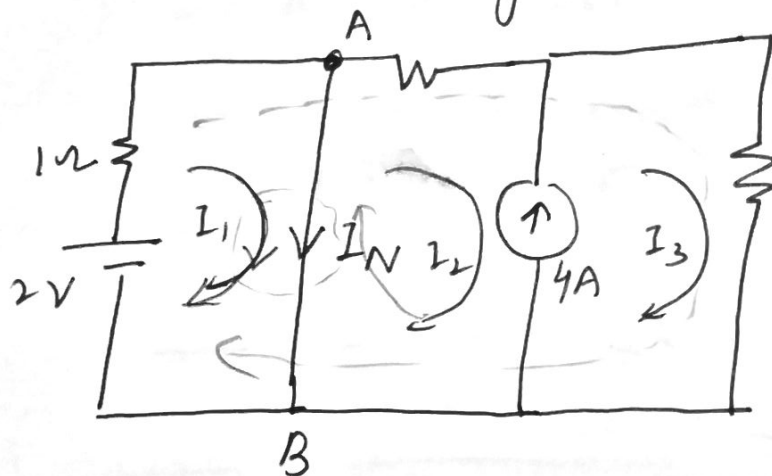

Using Mesh analysis w loop 1.

$$1I_1 - 2 = 0$$

$$\boxed{I_1 = 2A}$$

From the ckt it is clear that

$$\boxed{I_N = I_1 - I_2}$$

$$\& \boxed{4 = I_3 - I_2} \quad - (1)$$

Using KVL to super mesh.

$$5I_2 + 15I_3 + 2 + I_1 = 0$$

$$5I_2 + 15I_3 - 2 + 2 = 0$$

$$\boxed{5I_2 + 15I_3 = 0} \quad - (2)$$

After solving (1) & (2)

$$I_1 = 2A$$

$$I_2 = -3A$$


$$I_3 = 1A$$

$$\therefore I_N = I_1 - I_2$$

$$= 2 - (-3)$$

$$= 5A$$

Step II:- Calculation of R_{TH}

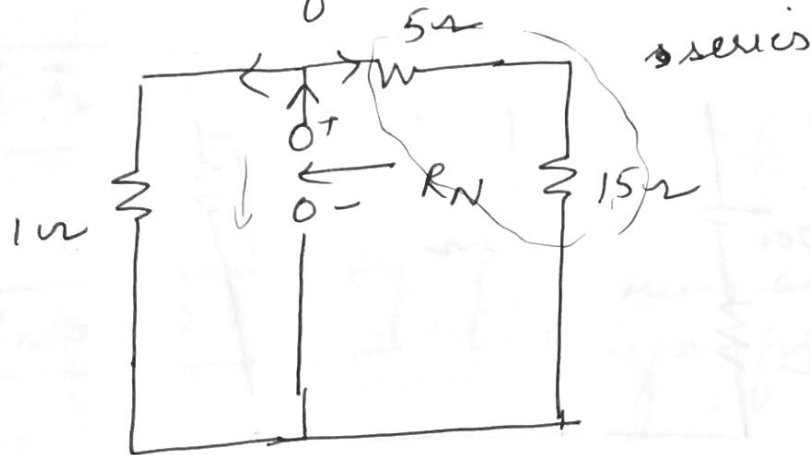

$$R_N = 1 \parallel (5 + 15)$$

$$R_N = 0.95\Omega$$

Step III:- Draw norton equivalent ckt




$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$

$$= \frac{0.95}{0.95 + 10} \times 5$$


$$I_L = 0.43A$$

Numerical - 2

Find the current through 10Ω res.

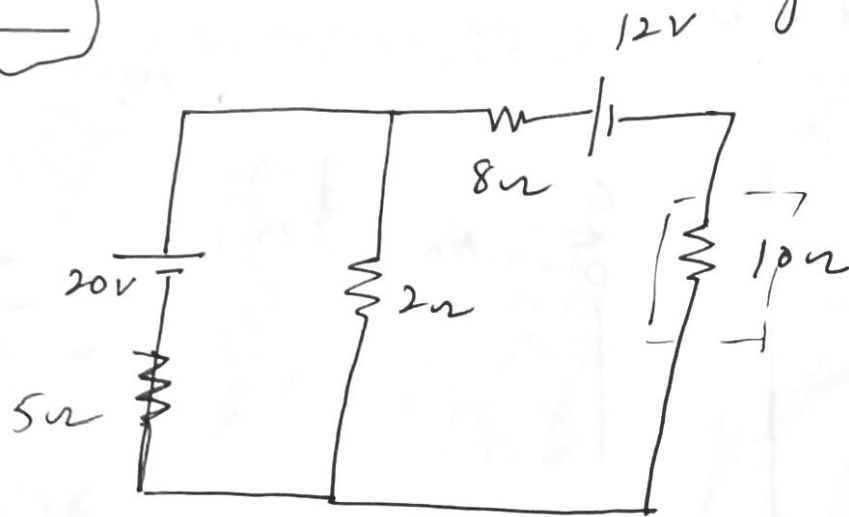

Solution:- Step 1:- Calculate I_N

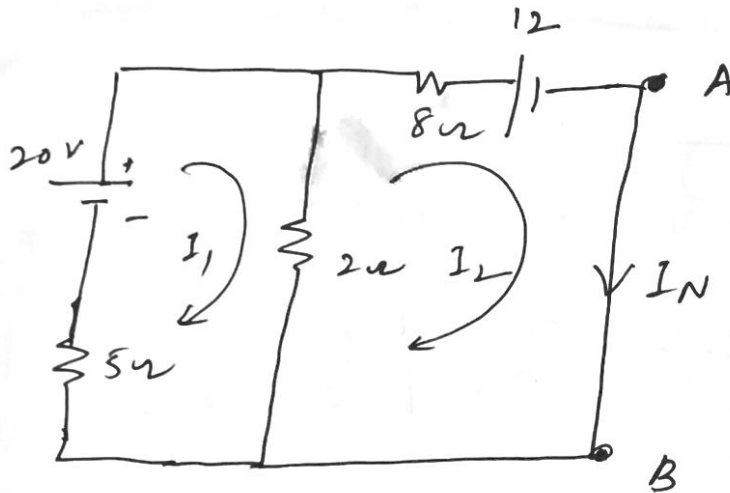

Using Mesh analysis in loop 1.

$$2(I_1 - I_2) + 5I_1 - 20 = 0$$

$$2I_1 - 2I_2 + 5I_1 - 20 = 0$$

$$\boxed{7I_1 - 2I_2 = 20} \quad \text{--- (1)}$$

$$8I_2 + 12 - 2(I_1 - I_2) = 0$$

$$8I_2 + 12 - 2I_1 + 2I_2 = 0$$

$$\boxed{10I_2 - 2I_1 = -12} \quad \text{--- (2)}$$

After solving ① & ②

$$I_2 = -0.67 \text{ A}$$

Now $I_2 = I_N$

$$\therefore I_N = -0.67 \text{ A}$$

[This means actually current is going from B to A]

Step III:-

Calculate R_N




$$R_N = (5 \parallel 2) + 8$$
$$= 9.43$$

Step IV:- Calculation of I_L


$$I_L = 0.67 \times \frac{9.43}{9.43 + 10}$$

$$= 0.33 \text{ A } (\uparrow)$$

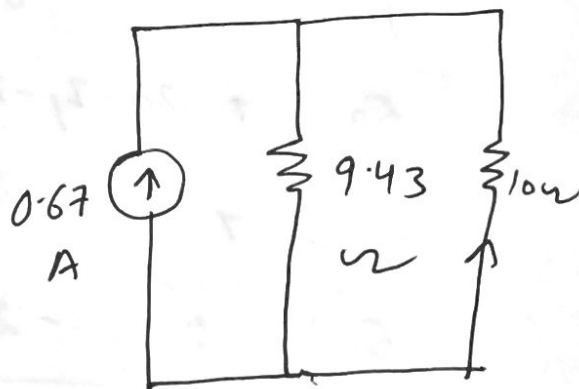


Numerical-3

Find the current in the 10Ω resistor

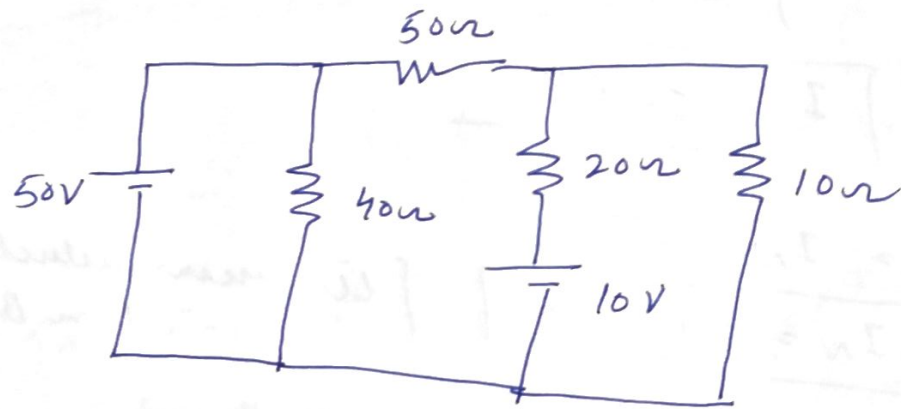

Solution:-

Step 1:- Calculation of I_N

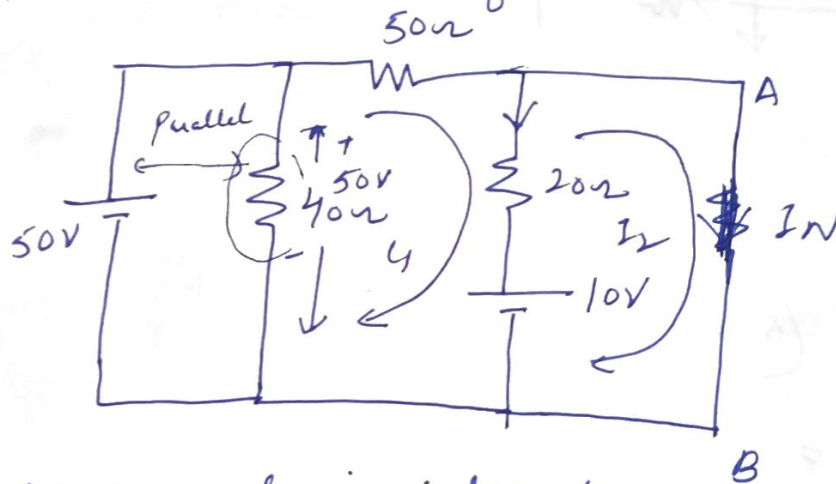

Using Mesh analysis in loop 1.

$$50I_1 + 20(I_1 - I_2) + 10 - 50 = 0$$

$$50I_1 + 20I_1 - 20I_2 - 40 = 0$$

$$50I_1 + 20I_1 - 20I_2 = 40$$

$$\boxed{70I_1 - 20I_2 = 40} \quad \text{--- (1)}$$

Applying Mesh analysis in loop 2.

$$-10 - 20(I_1 - I_2) = 0$$

$$\boxed{-20I_1 + 20I_2 = 10} \quad \text{--- (2)}$$

After solving = n ① ϵ ②

⑤


$$I_1 = 1A$$

$$I_2 = 1.5A$$

$$I_N = I_2 = 1.5A$$

Step II : Calculation of R_N

for short
ckt $R=0$

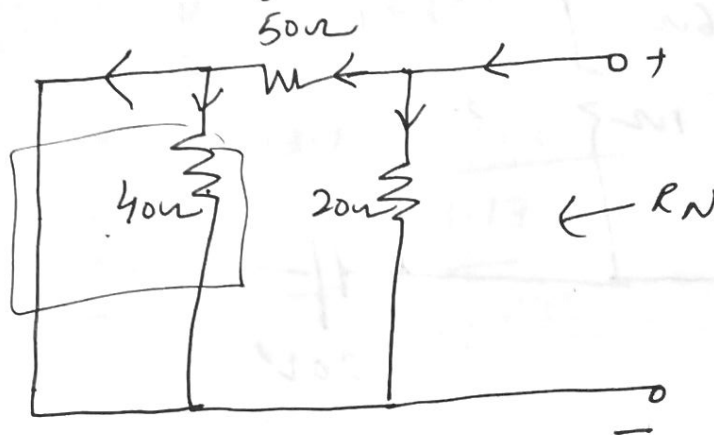


$$R_N = 40 \parallel 0 = 0$$

$$\therefore = 50 \parallel 20$$

$$R_N = 14.28\Omega$$


Step III : Calculation of I_L

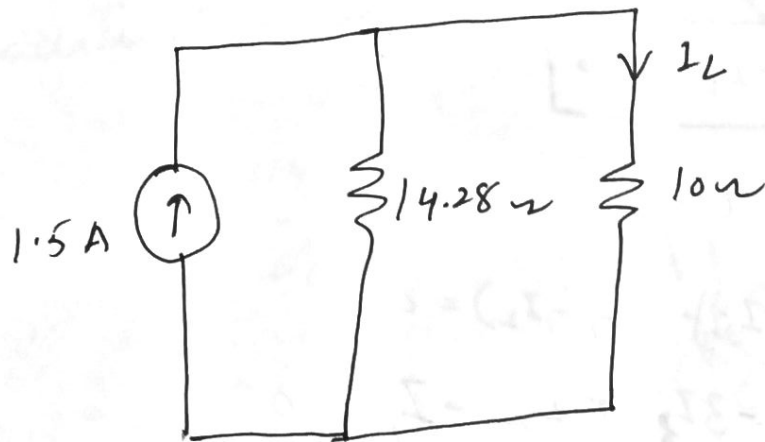


$$I_L = 1.5 \times \frac{14.28}{14.28 + 10}$$

$$= 0.88 \text{ A}$$

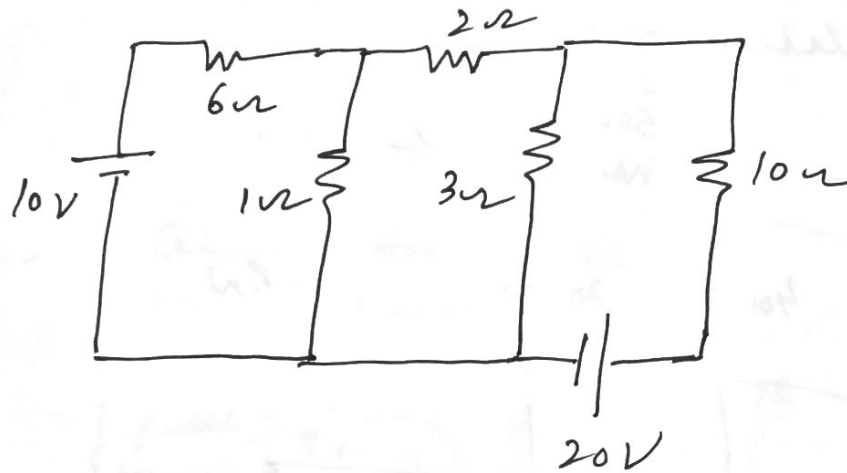Numerical-4 :- Find the current the 10Ω resistor.



Step-I :- Calculation of I_N

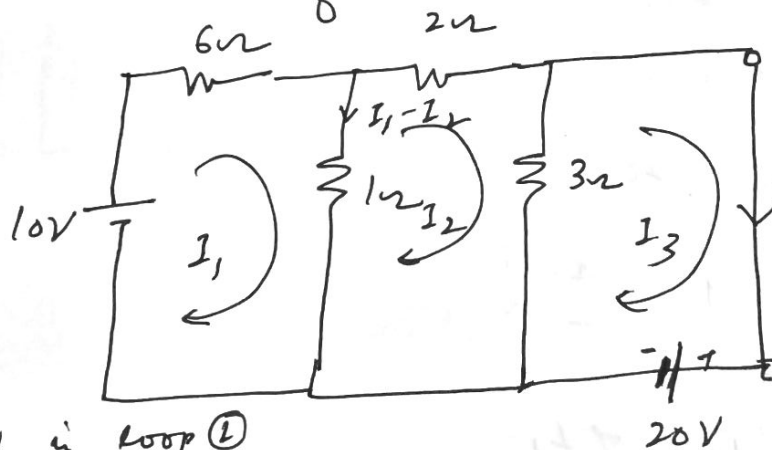

Applying KVL in loop ①
 $6I_1 + I_1 - I_2 - 10 = 0$

$$\boxed{7I_1 - I_2 = 10} \quad (1)$$

Applying KVL in loop ②
 $2I_2 + 3(I_2 - I_3) - (I_1 - I_2) = 0$

$$5I_2 - 3I_3 + I_2 - I_1 = 0$$

$$\boxed{6I_2 - I_1 - 3I_3 = 0} \quad (2)$$

Applying KVL to Mesh (3)

6

$$20 - 3(I_2 - I_3) = 0$$

$$-3I_2 + 3I_3 = -20$$

$$\boxed{3I_2 - 3I_3 = 20} \quad (3)$$

After solving = n (1), (2) & (3)

$$I_3 = -13.17 \text{ A}$$



$$\boxed{I_N = I_3 = -13.17 \text{ A}}$$

(that means current is going downward & upward)

Step II - Calculation of R_N

$$R_N = [6 || 1 + 2] || 3$$


$$= 1.46 \Omega$$

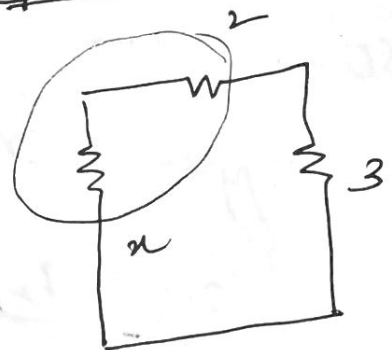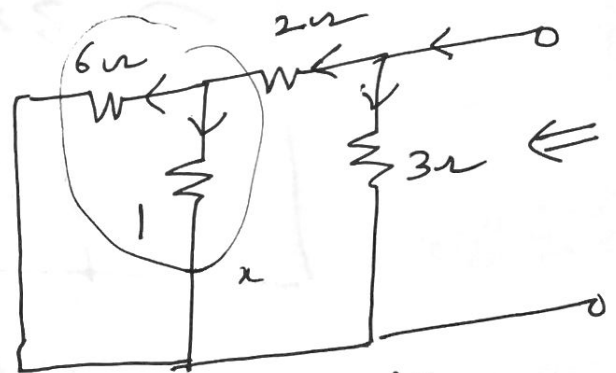

Step III - Calculation of I_L

$$I_L = \frac{13.17 \times 1.46}{1.46 + 10}$$


$$= 1.68 \text{ A}$$

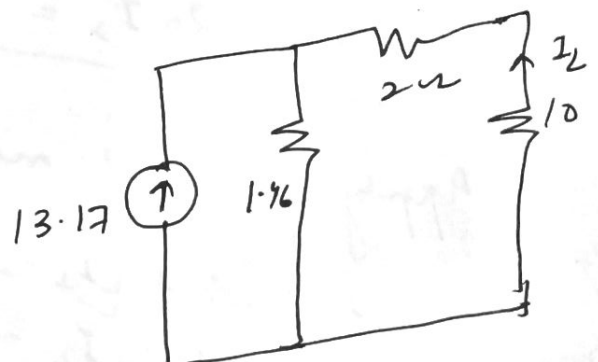


Numerical

5

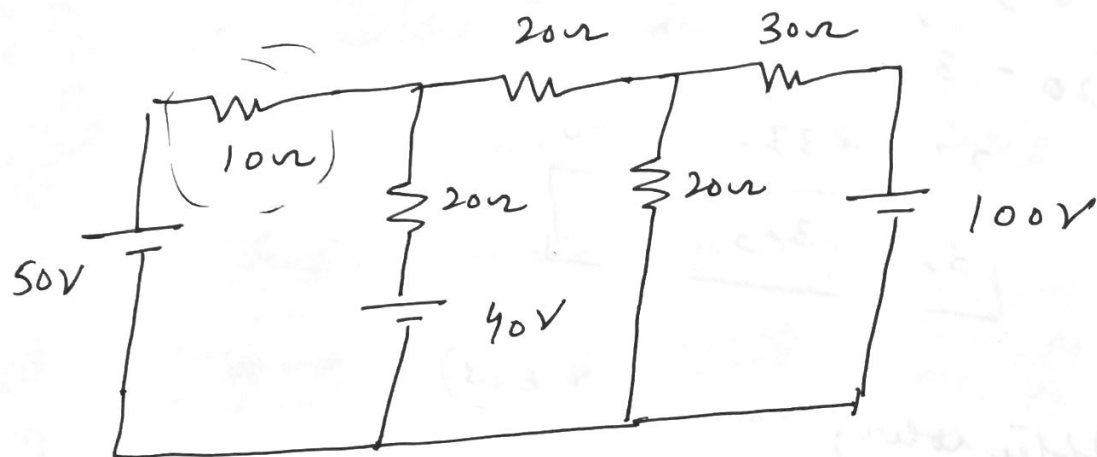Find the current through the 10Ω resistor



Solution:-

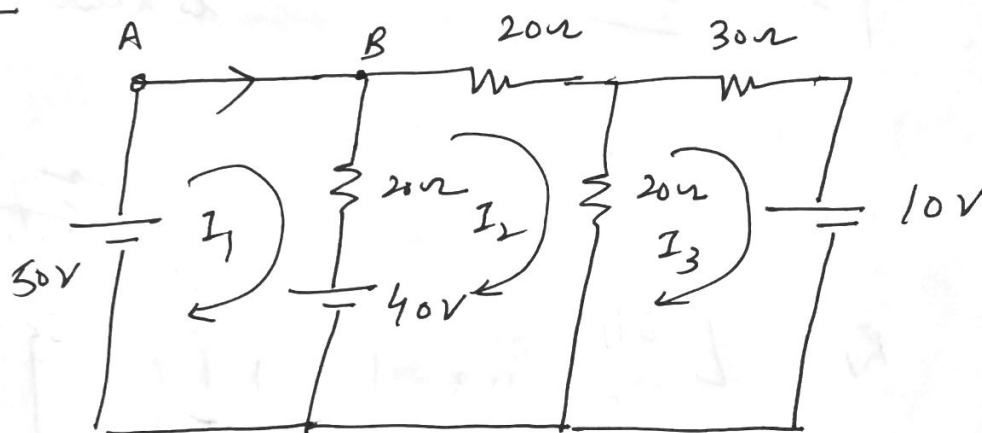

Step I calculation of I_N

Applying KVL to mesh 1

$$20(I_1 - I_2) + 40 - 50 = 0$$

$$\boxed{20I_1 - 20I_2 = 10} \quad \text{--- (1)}$$

Applying KVL to mesh (2)

$$20I_2 + 20(I_2 - I_3) - 40 - 20(I_1 - I_2) = 0$$

$$20I_2 + 20I_2 - 20I_3 - 40 - 20I_1 + 20I_2 = 0$$

$$\boxed{60I_2 - 20I_1 - 20I_3 = 40} \quad \text{--- (2)}$$

Applying KVL to Mesh 3

7

$$+20(I_2 - I_3) + 30I_3 + 100 = 0$$

$$-20I_2 + 20I_3 + 30I_3 = -100$$


$$\boxed{50I_3 - 20I_2 = 100} \quad \text{--- (3)}$$

After solving = (1), (2) & (3)

$$I_1 = 0.81 \text{ A}$$

$$\boxed{I_N = I_1 = 0.81 \text{ A}}$$

Step II :- Calculation of R_N

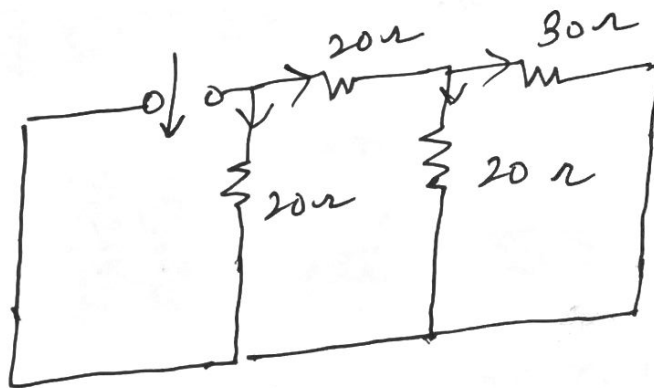

$$R_N = \left[(20 \parallel 30) + 20 \right] \parallel 20$$

$$= 12.3 \Omega$$

Step III :- Calculation of I_L

$$I_L = 0.81 \times \frac{12.3}{12.3 + 10}$$

$$= 0.45 \text{ A}$$