
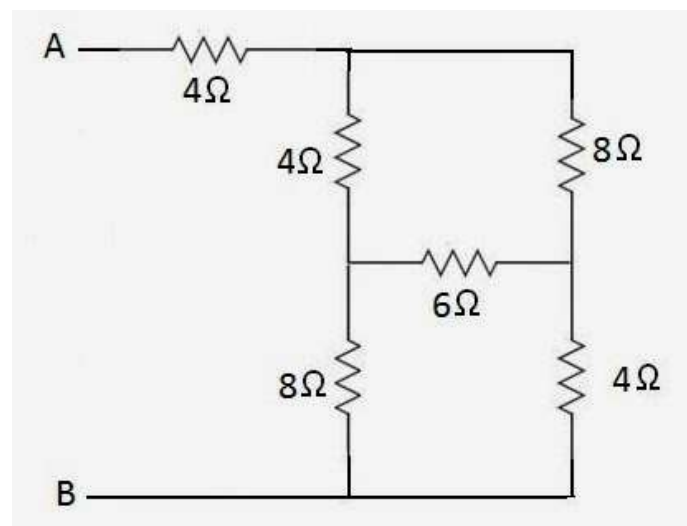


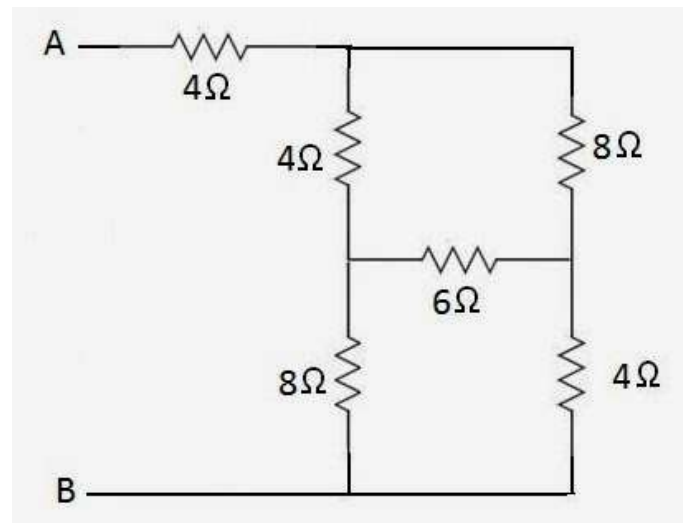- **Ques:- Find the equivalent resistance between A & B in the given network.**




- For the given network, we can easily determine the value of equivalent resistance i.e, R_{AB} through Star-Delta conversion.


We have



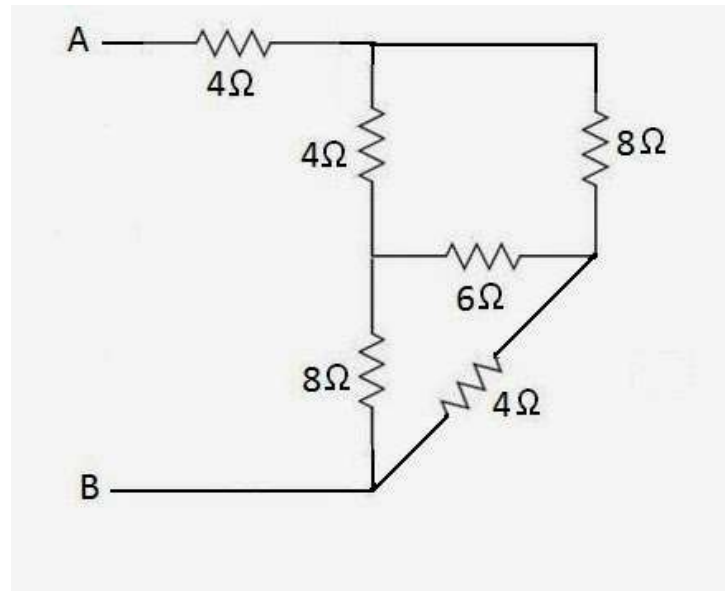Above network can also be represent as below:-



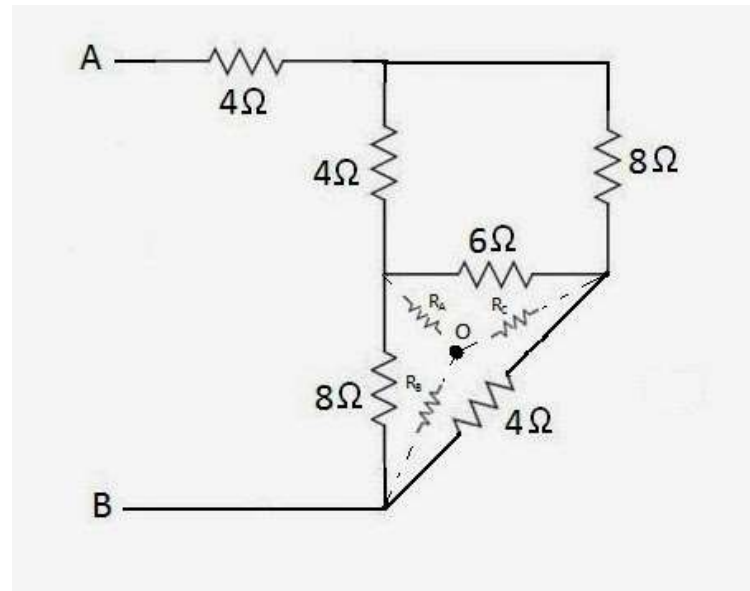Now, I am going to solved this network by using delta to star conversion as shown in the figure given below:-





For the value of new star connected resistance are finding through direct formula of [delta to star conversion](#), as shown below

$$R_A = \frac{8 \cdot 6}{8 + 6 + 4}$$
$$R_A = 2.66\Omega$$


$$R_B = \frac{8 \cdot 4}{8 + 6 + 4}$$
$$R_B = 1.77\Omega$$
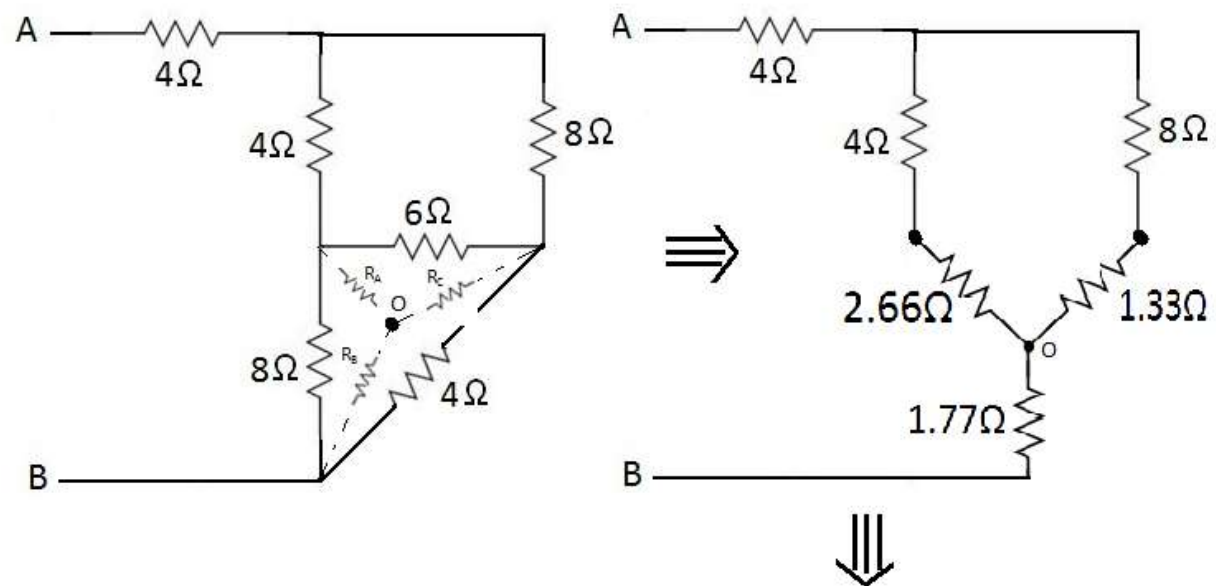
$$R_C = \frac{6 \cdot 4}{8 + 6 + 4}$$
$$R_C = 1.33\Omega$$



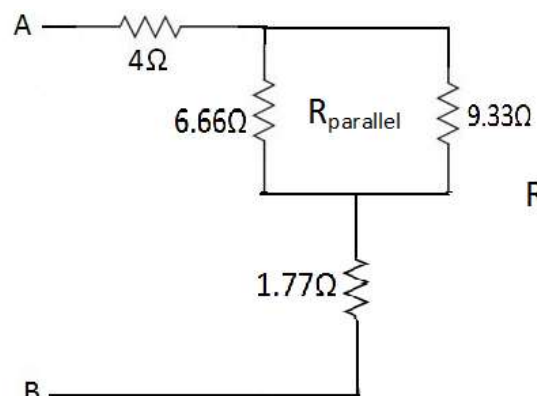
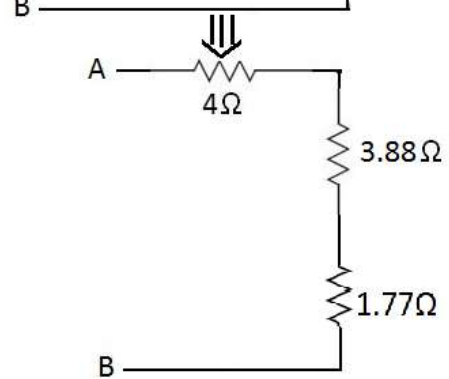
$$R_{\text{parallel}} = \frac{6.66 \times 9.33}{6.66 + 9.33} = 3.88\Omega$$



- so, R_{AB} or $R_{\text{equivalent}} = R_1 + R_2 + R_3 = 4\Omega + 3.88\Omega + 1.77\Omega = 9.65\Omega$ Answer