

# Basics of Electric Circuit

BY :MANKIRAN KAUR

# CONTENTS

- BASICS OF ELECTRIC CIRCUIT, voltage and current sources, Kirchhoff's current and voltage laws



## Electric Circuit

- The system in which electric current can flow from source to load through one path and after delivering energy at load, the current can return to the other terminal of source through another path is referred as electric circuit.


# voltage and current sources

## Main Parts of an Electric Circuit

- Electrical Sources (for delivering electricity to the circuit and these are mainly electric generators and batteries)
- Controlling Devices (for controlling electricity and these are mainly switches, circuit breakers, **MCBs** etc.)
- Protection Devices (for protecting the circuit from abnormal conditions and these are mainly **electric fuses**, **MCBs**, Switchgear systems)
- Conducting Path (to carry current one point to other in the circuit and these are mainly wires or conductors)
- Load

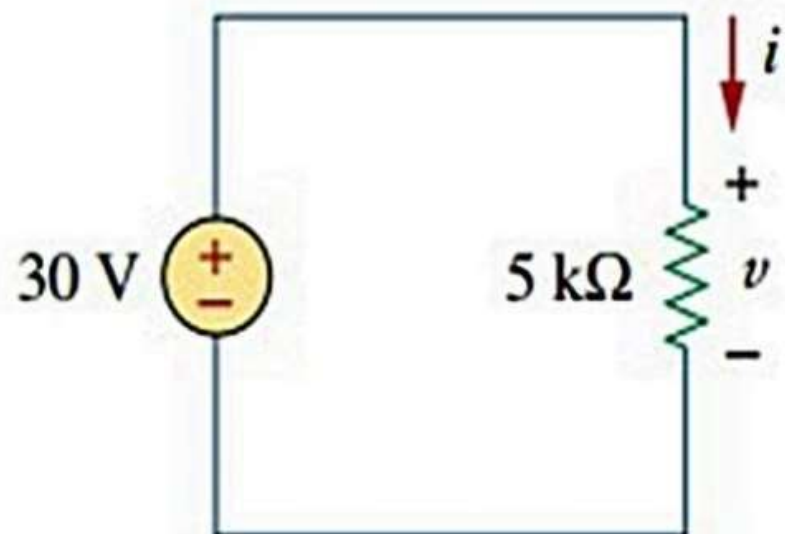
## Basic Properties of an Electric Circuit

- A circuit is always a closed path.
- A circuit always contain an energy source which acts as source of electrons.
- The electric elements include uncontrolled and controlled source of energy, resistors, capacitors, inductors, etc.
- In an electric circuit flow of electrons takes place from negative terminal to positive terminal.
- Direction of flow of conventional current is from positive to negative terminal.
- Flow of current leads to potential drop across the various elements.



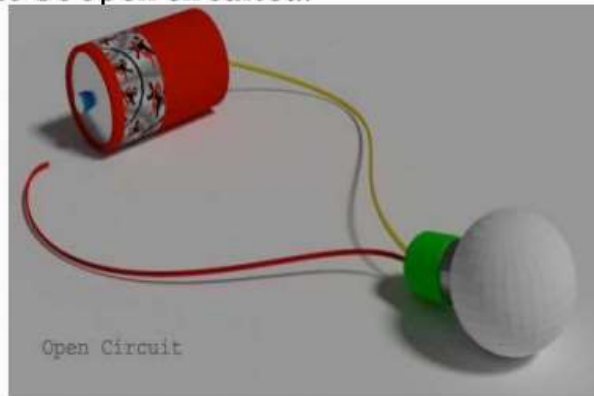
## Types of Electric Circuit

- **Open Circuit**-If due to disconnection of any part of an electric circuit if there is no flow of current the circuit is said to be open circuited.



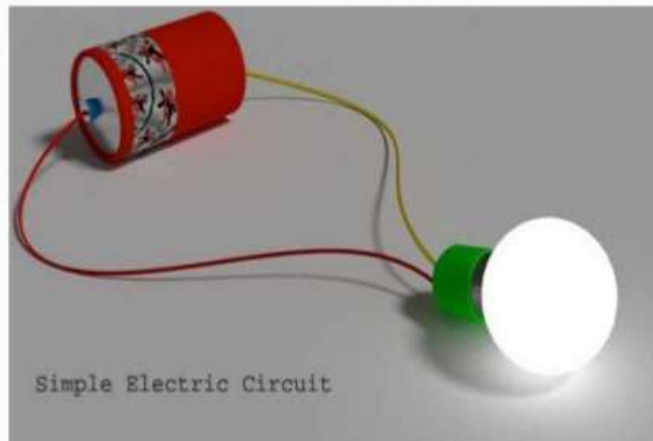- **Closed Circuit**-If there is no discontinuity in the circuit and current can flow from one part to another part of the circuit then the circuit is said to be closed circuit.







Electric circuits can further be categorized according to their structural features.

- Series Circuit
- Parallel Circuit
- Series Parallel Circuit.






## Passive Components

- The element which receives energy (or absorbs energy) and then either converts it into heat or stores it in an electric or magnetic field called **Passive Element**.

**Example:** Resistor, Inductor, Capacitor etc.

## Passive Components

Component	Symbol	Basic Measure (Unit)
Resistor		Ohm ( $\Omega$ )
Inductor		Henry (H)
Capacitor		Farad (F)

# CURRENT

- Current is Defined as the Flow of the Electric Charge..
- Current is Basically Denoted by Symbol **I**.
- The Unit for the Current is **A** or ampere.
- SI Unit of Current is **Coulomb/Second**
- Measuring Element used for Current is Ammeter.

## VOLTAGE



- Voltage is a Potential Difference between Two Points of an Electrical Field.
- It is Denoted by Symbol **V**
- The Unit for Measurement of Voltage is **Volts**.
- SI Unit for Voltage is **Joule/Coulomb**
- Measuring Element for Voltage is Voltmeter.

## Energy Sources

- According to the Terminal Voltage-Current Characteristics, Electrical energy Sources are Categorized into two Parts.
  1. Voltage Source
  2. Current Source

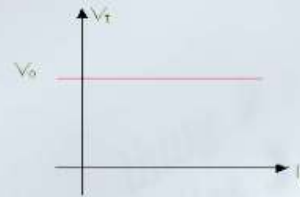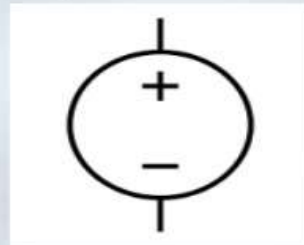
## VOLTAGE SOURCE

- The Voltage Source is a Two Terminal Element in which the Voltage is completely independent of the Current.




- The Representation of Voltage Source is Done by the Fig Shown Above.


## Different Voltage Sources

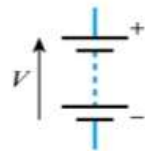

(a) A battery

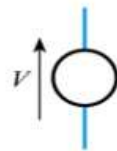


(b) An ideal voltage source

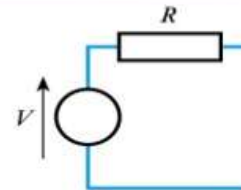

(c) Modelling a battery using an ideal voltage source



(d) An alternating voltage source

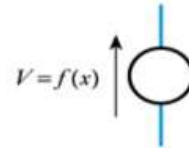

(e) A controlled voltage source



## Facts about Voltage Source

- A Voltage source produces an **Electromotive Force (e.m.f.)** which causes a current to flow within a circuit
  - Unit of e.m.f. is the **volt**
  - a volt is the potential difference between two points when a joule of energy is used to move one coulomb of charge from one point to the other
- Real voltage sources, such as batteries have resistance associated with them
  - In analysing circuits we use **Ideal Voltage sources**
  - we also use **controlled** or **dependent Voltage sources**

## OHM's Law

- The Relationship between Voltage and Current is Given by OHM's Law.

$$V \propto I$$

- Constant of Proportionality is Resistance R  
Hence


$$V = IR \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

- Current through a Resistor causes power dissipation

$$P = IV \quad P = \frac{V^2}{R} \quad P = I^2 R$$
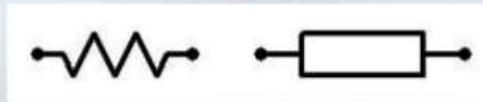
## Resistors

- The Components used to Oppose the Flow of Current through it is Called **Resistor**.



- And the Property of a Material to Oppose Current is called **Resistance**.


# Law of Current

- *At any instant, the algebraic sum of all the currents flowing into any node in a circuit is zero*
- If currents flowing *into* the node are positive, currents flowing *out of* the node are negative, then  $\sum I = 0$


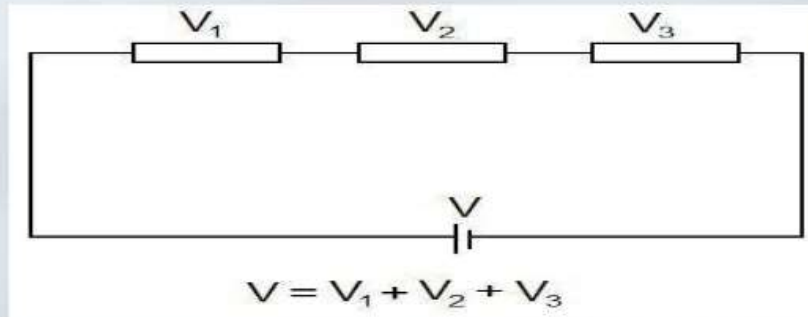
## Law of Voltage

- *At any instant the algebraic sum of all the voltages around any loop in a circuit is zero*
- If clockwise voltage arrows are positive and anticlockwise arrows are negative then  $\Sigma V = 0$



# Kirchoff's law

- Kirchhoff's current law (1st Law) states that current flowing into a node (or a junction) must be equal to current flowing out of it. This is a consequence of charge conservation.
- Kirchhoff's voltage law (2nd Law) states that the sum of all voltages around any closed loop in a circuit must equal zero. This is a consequence of charge conservation and also conservation of energy.

# Kirchoff's current law

- Current flow in circuits is produced when charge carriers travel through conductors. Current is defined as the rate at which this charge is carried through the circuit. A fundamental concept in physics is that charge will always be conserved. In the context of circuits this means that, since current is the rate of flow of charge, the current flowing into a point must be the same as current flowing out of that point.

# KIRCHOFFS LAW

## CURRENT ELECTRICITY.

### \* KIRCHHOFF'S CURRENT LAW.

"The algebraic sum of all the current at a junction in a closed circuit is always zero."

$$\sum I_{\text{junction}} = 0$$

law of conservation of charge

#### Sign Convention

Incoming current = +ve  
outgoing current = -ve



$$I_1 + I_2 + I_3 - I_4 - I_5 = 0$$

$$I_1 + I_2 + I_3 = I_4 + I_5$$

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

Eg:-



at x

$$I_1 + 2 = I_2$$

at y

$$I_2 = 2 + 3 = 5A$$

at z

$$3 + 1 = I_3$$

$$I_3 = 4A$$

$$I_1 = 3A$$



# CURRENT ELECTRICITY.

## KIRCHHOFF'S VOLTAGE LAW.


In a closed circuit, algebraic sum of all emf and potential drop in a loop is equal to zero.

$$\sum (E + IR)_{\text{loop}} = 0$$


Law of conservation of energy.

### SIGN CONVENTION


For Cell:-

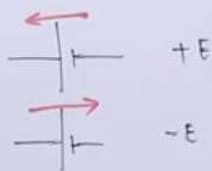

For Potential drop:-

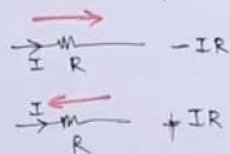

Example:-

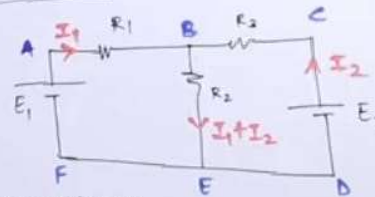

In loop ABEFA

$$-I_1 R_1 - R_2 (I_1 + I_2) + E_2 = 0 \quad \text{--- (1)}$$

In loop BCDEB

$$+I_2 R_3 - E_2 + R_2 (I_1 + I_2) = 0 \quad \text{--- (2)}$$

In loop ABCDEFA

$$-I_1 R_1 + I_2 R_3 - E_2 + E_1 = 0 \quad \text{--- (3)}$$

# quiz

Kirchhoff's First  
Law says that:



Current loses strength as it flows about a circuit



Voltage loses strength as it flows about a circuit



Wires need insulation to stop electrons from leaking out of the wire



Total current flowing into a point is the same as the current flowing out of that point

Question 1

## Question 2



KCL is used when solving circuits with...



Closed loops

Sufficient nodes/ junctions

Capacitors

None



If a circuit contains three loops, how many *independent* equations can be obtained with Kirchhoff's Second laws?



Three



Four




Five



Six

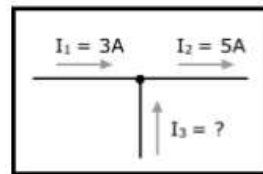Question 5

➔ How much is current  $I_3$  in the node shown?



2A



-2A



0A




8A

Question 6
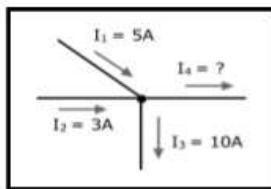
## Question 7



How much is current  $I_4$  in the node shown?



2A



-2A



18A




8A

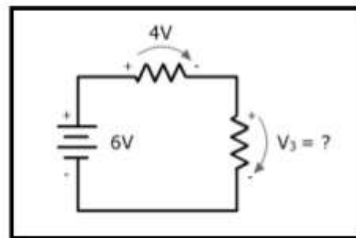QUESTION  
8



How much is voltage  $V_3$  in the closed loop circuit shown?



2A



-2A




10A



-10A



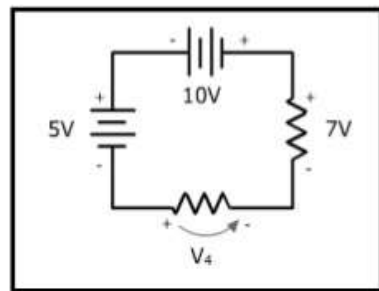How much is voltage  $V_4$  in the closed loop circuit shown?



4A



-4A



8A



-8A

