

Electric Circuits and Networks

-----BASICS-----

By:mankiran kaur


OVERVIEW

- What's
 - Voltage
 - Current
 - Energy
 - Power
- Network Elements
- Parameters of Electric circuit
- Conclusion

VOLTAGE

- Always a force of attraction exists between +ve and -ve charges in an atom.
- The energy required to overcome this force and move the charge through specific distance is called potential energy.
- The difference in Potential Energy is called **Potential Difference (Electrical term: VOLTAGE)**
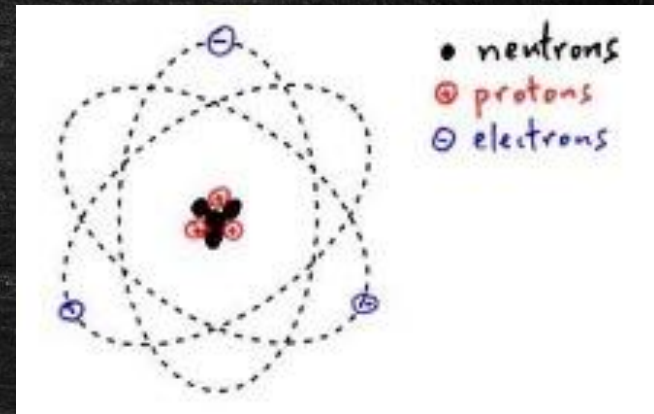
$$V = \frac{W \text{ (energy)}}{Q \text{ (Charge)}}$$




CURRENT


- The rate of flow of electrons in a conductive or semiconductive material.
- It is measured by the number of electrons flow past a point in unit time.

$$I = \frac{Q(\text{Charge})}{t(\text{time})}$$

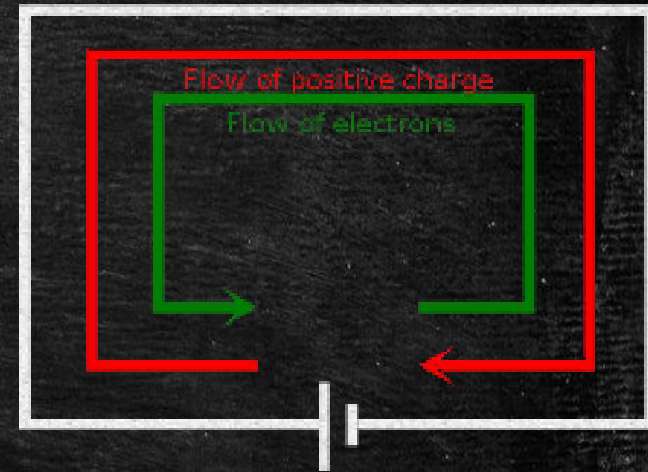NOTE: $1\text{A} = 1\text{COULOMB/sec} = 6.25 \times 10^{28} e^{-}\text{s/sec}$



ANALOGY

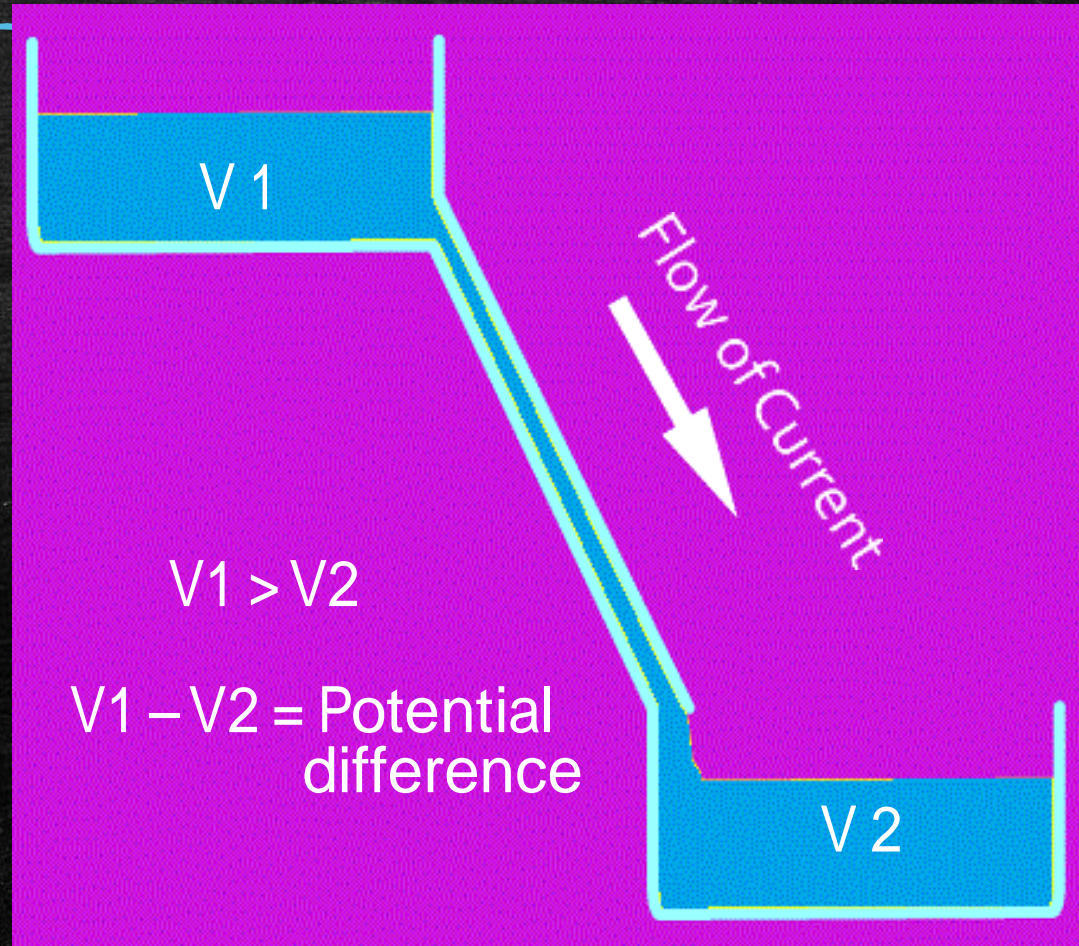

Energy and Power

- Energy - Capacity for doing work
(measured in terms of **Joules**)
- Power - Rate of change of energy in unit time
(measured in terms of **Watts**)

$$P = \frac{W \text{ (Energy)}}{t \text{ (time)}}$$

Note : **1W = 1J / Sec**

NETWORK ELEMENTS

We can classify network elements into 4 types:

1. Active / Passive Elements
2. Bilateral / Unilateral Elements
3. Linear / Non-Linear Elements
4. Lumped / Distributed Elements

ACTIVE AND PASSIVE ELEMENTS

The Active elements have the capability to deliver average power greater than zero for infinite period of time to the connected devices.


Eg: Ideal power sources, Battery, etc.,



Passive elements = $\text{Active elements}^{-1}$

It consumes or dissipate the energy stored in the circuit.

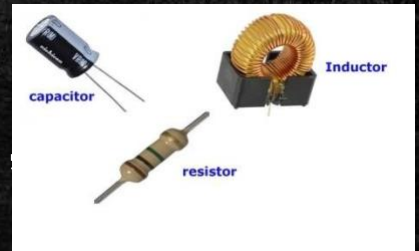Eg: Resistors, Inductors, Capacitors, etc.




BILATERAL AND UNILATERAL

- The bilateral elements have same V-I relationship for current flow in either direction.

Eg : Any conducting wire, Resistors.



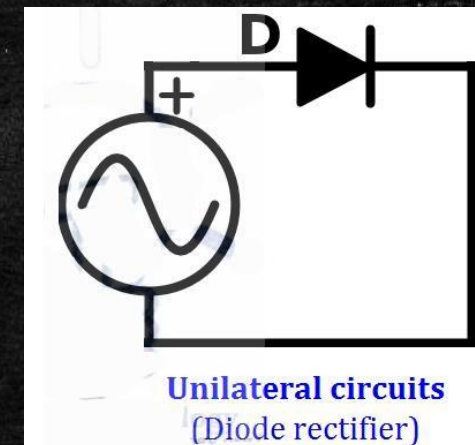- Unilateral Elements = Bilateral elements⁻¹
- Eg : Vacuum diodes, Silicon diodes, rectifiers, etc.,



LINEAR AND NON-LINEAR

- Linear elements have linear V-I relationship (i.e. Straight line) passing through origin.
- Linear elements obeys superposition theorem.

Eg: Resistors

- Non-Linear Elements = $\text{Linear elements}^{-1}$

Eg: SCR, Triac


LUMPED AND DISTRIBUTED

- Small in size and simultaneous action takes place for any given cause at same time of instant.

(size is very small compared to wavelength of signal applied) Eg: R,L,C

- Distributed Elements are not electrically separable for any analytical purpose.

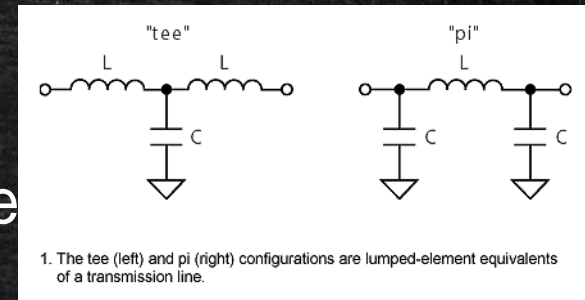Eg: Transmission line has its distributed R,L,C throughout its entire length.




PARAMETERS

- Three major parameters used in an electric circuits are
 1. Resistance
 2. Inductance
 3. Capacitance


RESISTANCE

$$R = 0\Omega$$

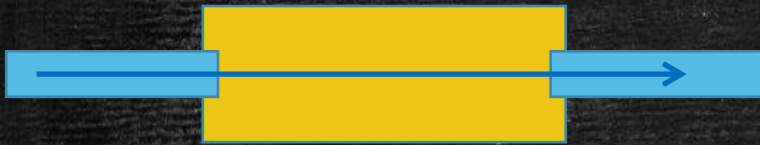

- No more collision for electrons within the material
- Free flow of current (No drop)


$$R \neq 0\Omega$$

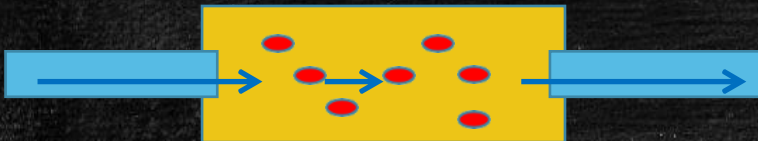

- Due to physical property of material, collision of electrons with atoms of material takes place.
- The flow of current is resisted by value R
- Drop in potential across material

INDUCTANCE

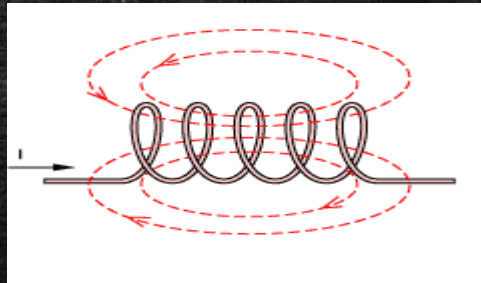- A wire of certain length is twisted into coil to form a basic inductor.



For larger 'I' more flux develops around coil

When 'I' changes instantaneously, flux also changes. According to faraday's law some voltage is induced, and it is given by


$$V = L \frac{di}{dt}$$

Note: For DC, $\frac{di}{dt} = 0$. Hence $V = 0$. (Short circuit)

CAPACITOR

- It has two conducting surfaces separated by dielectric.
- Capacitance is the amount of charge a capacitor can store when a voltage is applied across it.

$$C = \frac{Q}{V}$$

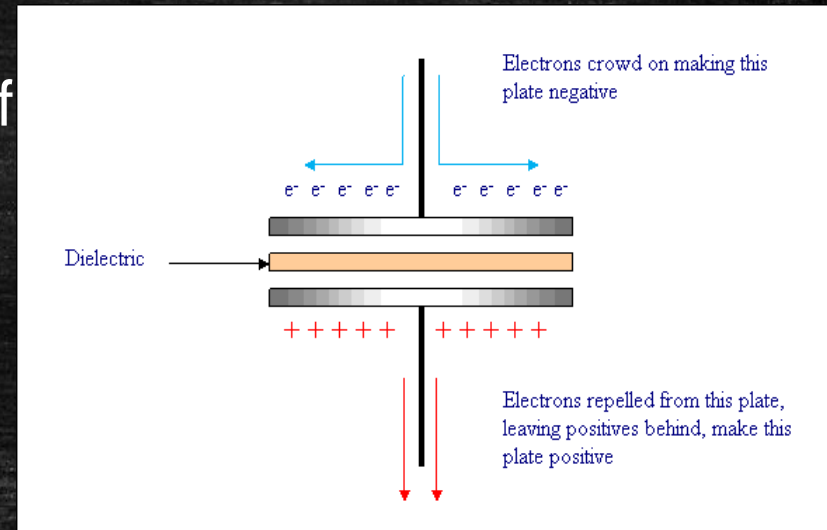

The simple
presentation
ends here

And finally, It's time to

